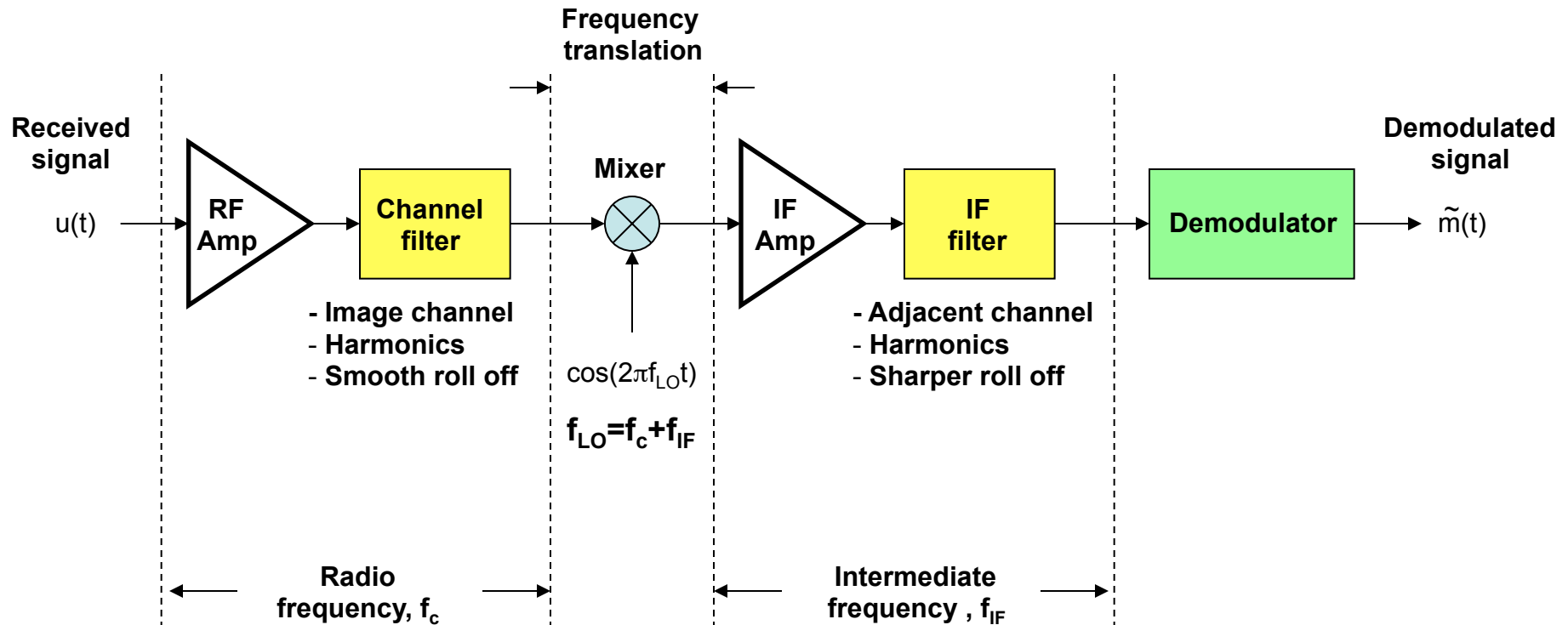



# **Super-heterodyne receiver: Notes and MATLAB demo**

# The super-heterodyne receiver






**NOTE:** Selecting  $f_{LO} = f_c - f_{IF}$  results in an **infra-heterodyne** receiver

# Image channel problem

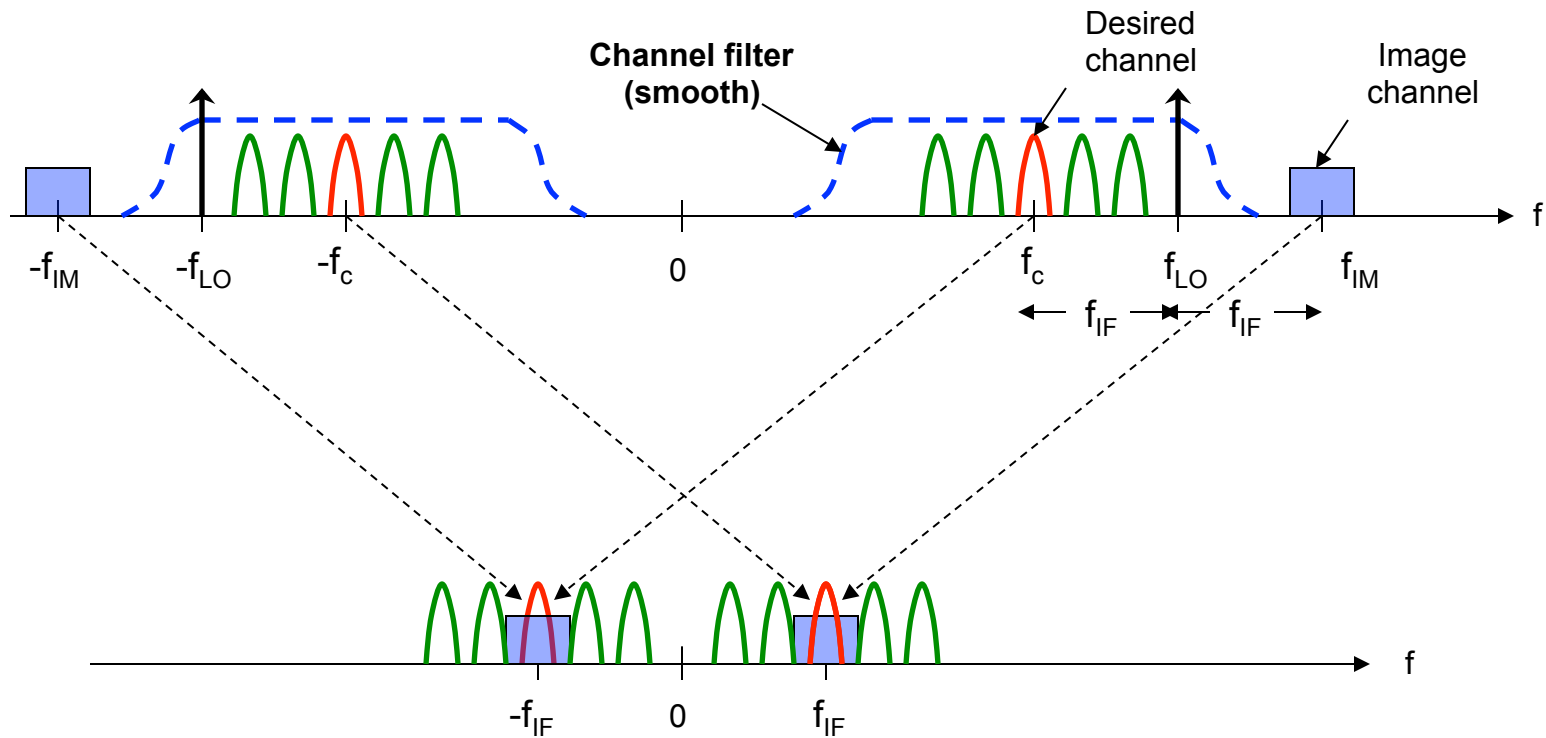


# IF filter characteristics

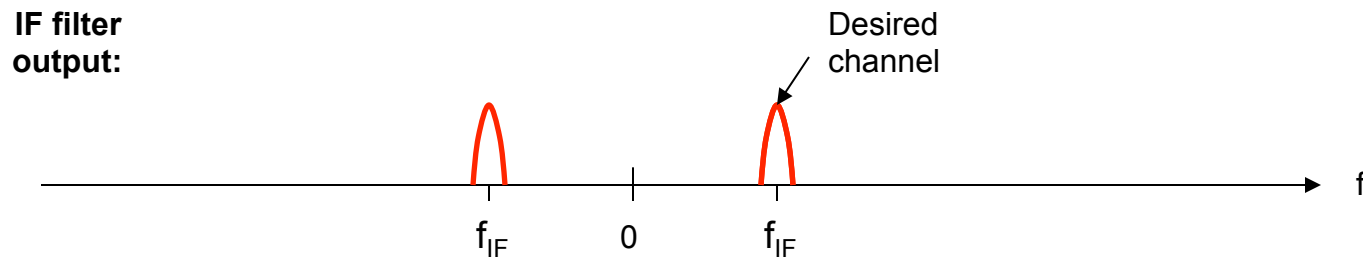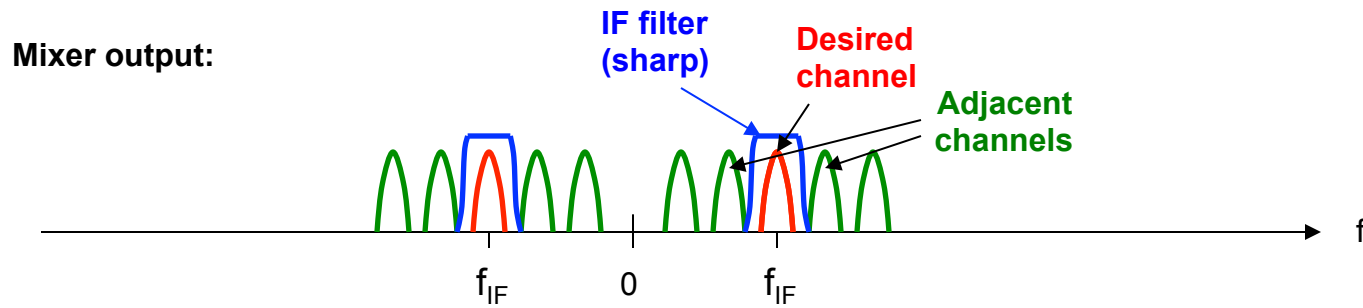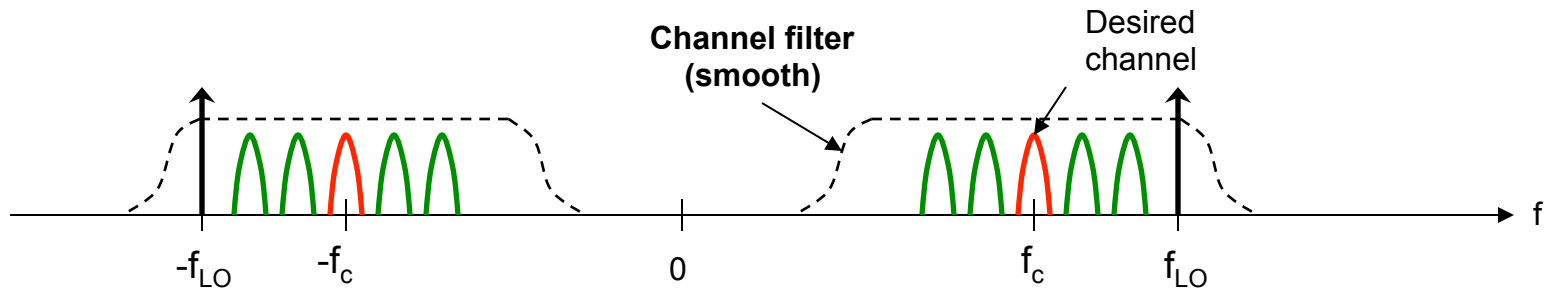
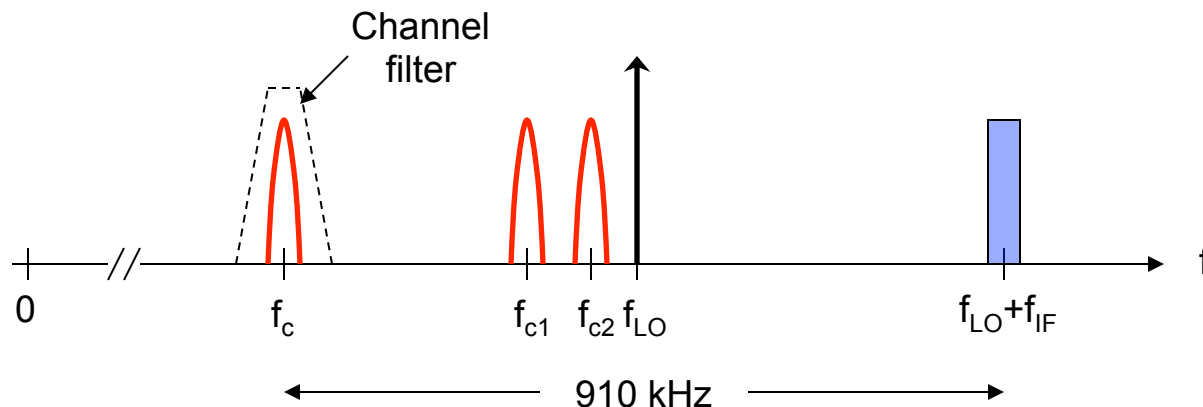
# MATLAB demo

- Desired channel (3 KHz sinusoidal):  $f_c = 560$  kHz ( $B=10$  kHz)
- $f_{IF} = 455$  kHz
- $f_{LO} = 1015$  kHz



- Two in-band channels:  $f_{c1}=920$  kHz,  $f_{c2}=960$  kHz (both  $B=10$  kHz)
- One image channel (sawtooth waveform) at  $f_{IM}=f_{LO}+f_{IF}=1470$  kHz
- The channel filter ( $B=20$  kHz) can be set on and off via a manual switch in the model